
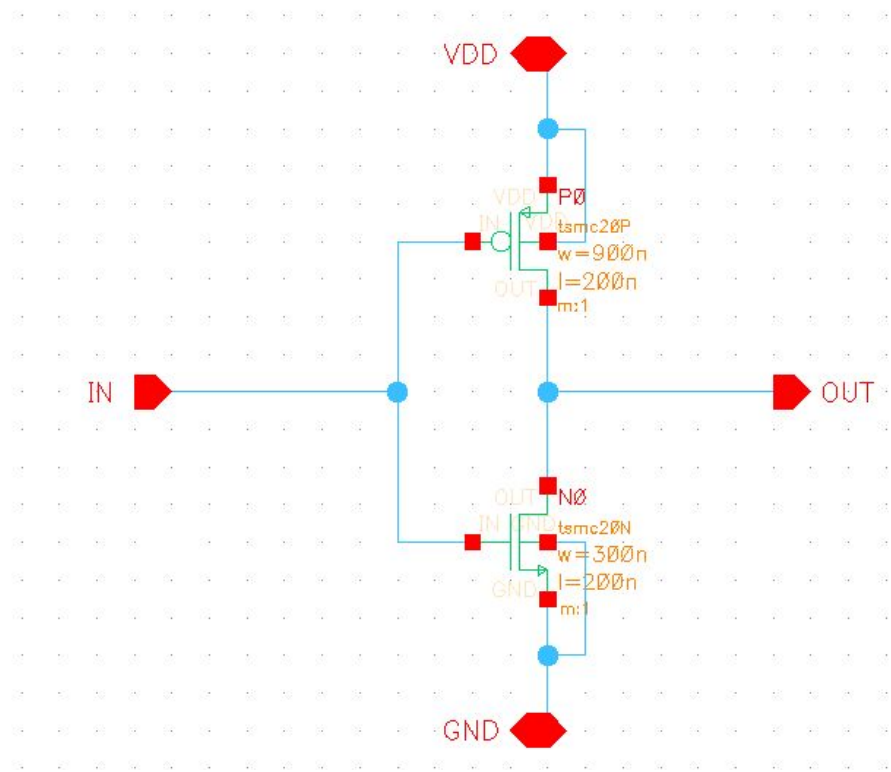



Inverter Schematic

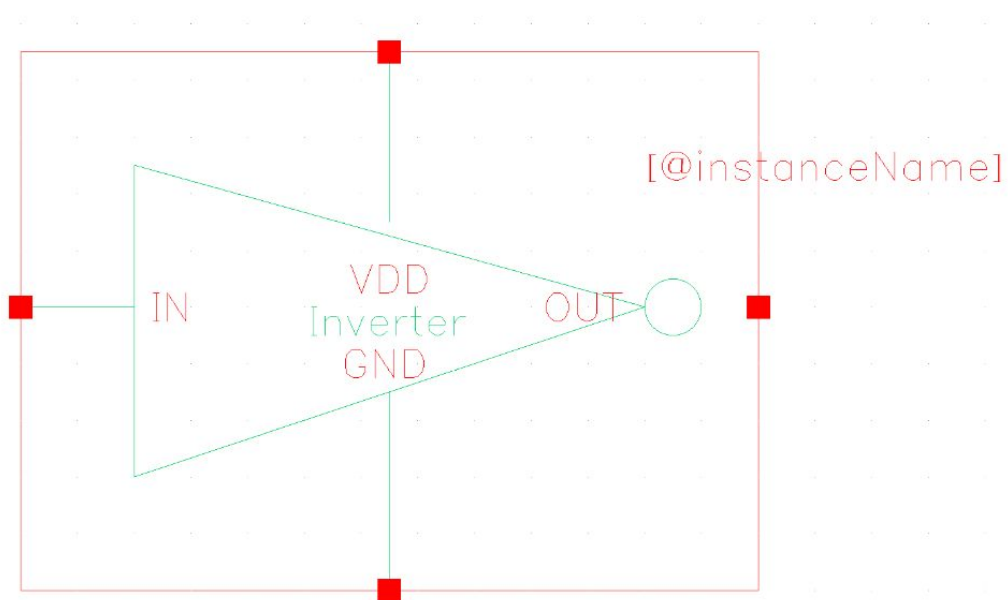


Inverter Symbol



Inverter Layout

 

Inverter Extracted

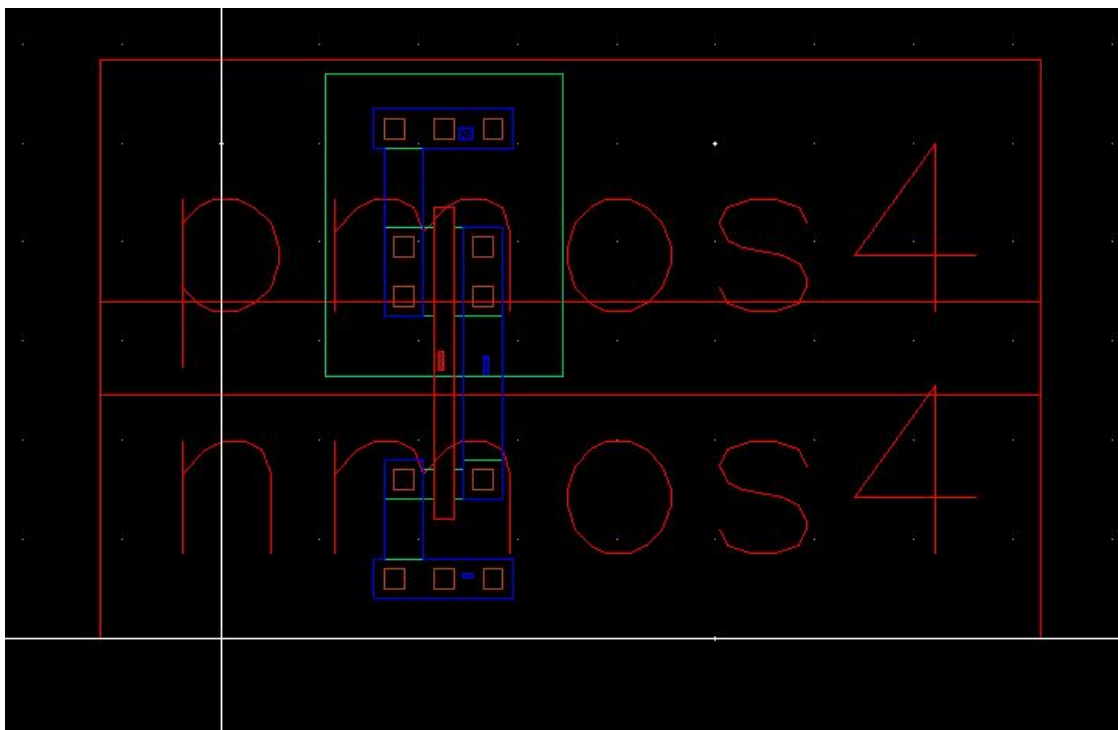

Inverter LVS output file

Command line: /opt/coe/cadence/IC618/tools.lnx86/dflII/bin/64bit/LVS -dir /home/ugrads/k/khoadiep/LVS -l -s -t /home/ugrads/k/khoadiep/LVS/layout /home/ugrads/k/khoadiep/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/ugrads/k/khoadiep/LVS/layout/netlist

count	
4	nets
4	terminals
1	pmos
1	nmos

Net-list summary for /home/ugrads/k/khoadiep/LVS/schematic/netlist

count	
4	nets
4	terminals
1	pmos
1	nmos

Terminal correspondence points


N0	N1	GND
N2	N0	IN
N1	N3	OUT
N3	N2	VDD

Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4


The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	2	2
total	2	2
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	4	4
total	4	4
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	4	4


NAND Schematic

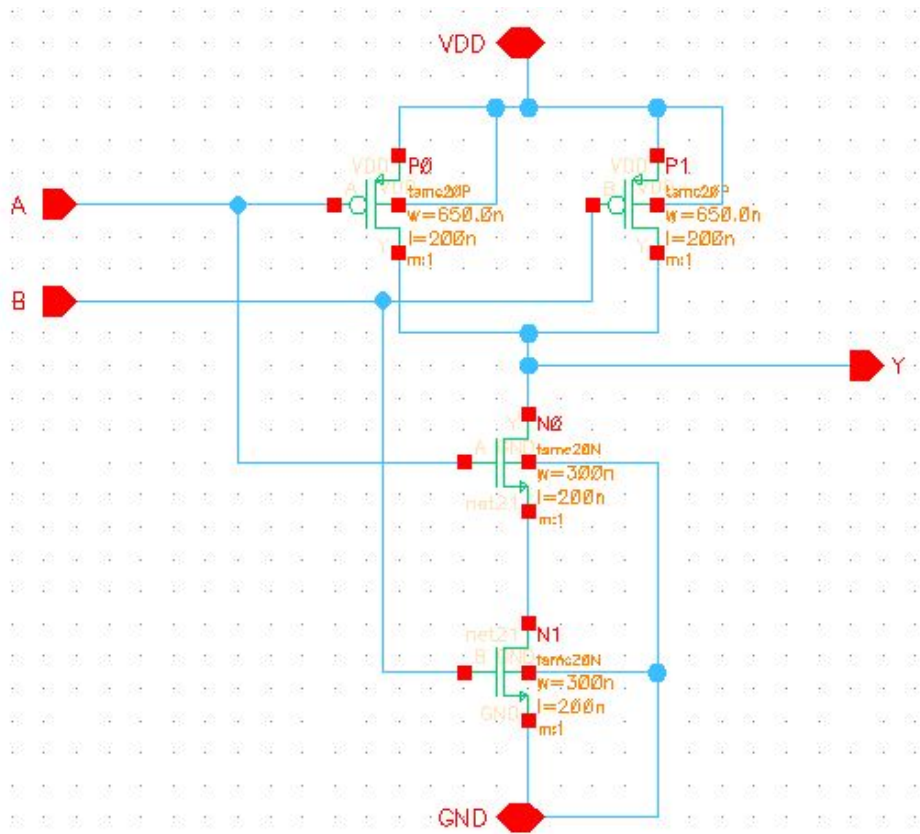


NAND Symbol

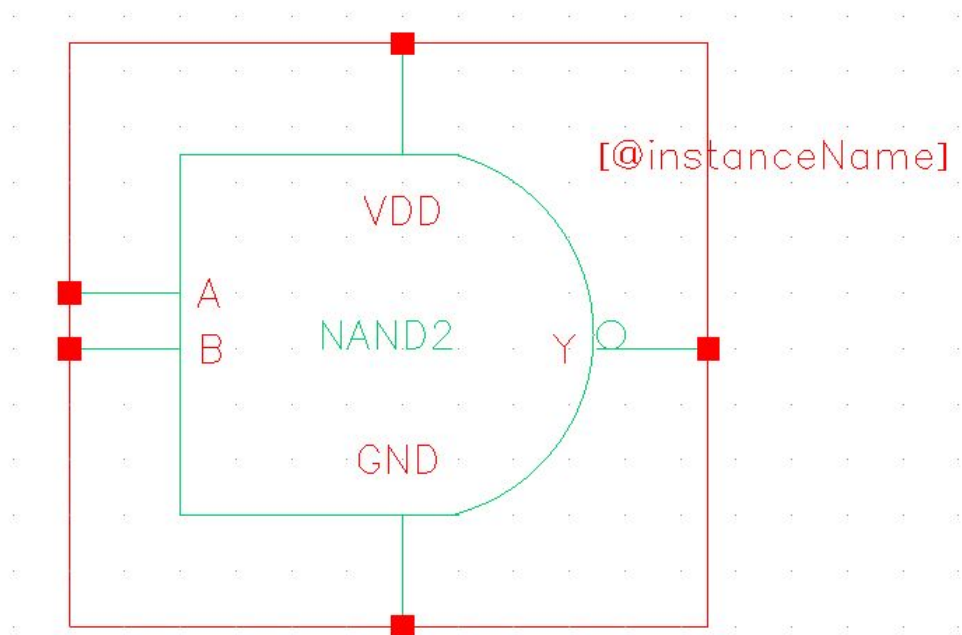

NAND Layout

 

NAND Extracted

 

NAND LVS output file

```
Command line: /opt/coe/cadence/IC618/tools.lnx86/dftII/bin/64bit/LVS -dir /home/ugrads/k/khoadiep/LVS -l -s -t /home/ugrads/k/khoadiep/LVS/layout /home/ugrads/k/khoadiep/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling Diva LVS rules...

Net-list summary for /home/ugrads/k/khoadiep/LVS/layout/netlist
count
6      nets
5      terminals
2      pmos
2      nmos

Net-list summary for /home/ugrads/k/khoadiep/LVS/schematic/netlist
count
6      nets
5      terminals
2      pmos
2      nmos

Terminal correspondence points
N4      N1      A
N3      N5      B
N2      N0      GND
N5      N4      VDD
N1      N2      Y

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.


          layout schematic
          instances
un-matched      0      0
rewired          0      0
size errors     0      0
pruned          0      0
active          4      4
total           4      4

          nets
un-matched      0      0
merged          0      0
pruned          0      0
active          6      6
total           6      6


          terminals
un-matched      0      0
matched but
different type   0      0
total           5      5

Probe files from /home/ugrads/k/khoadiep/LVS/schematic
```


XOR Schematic

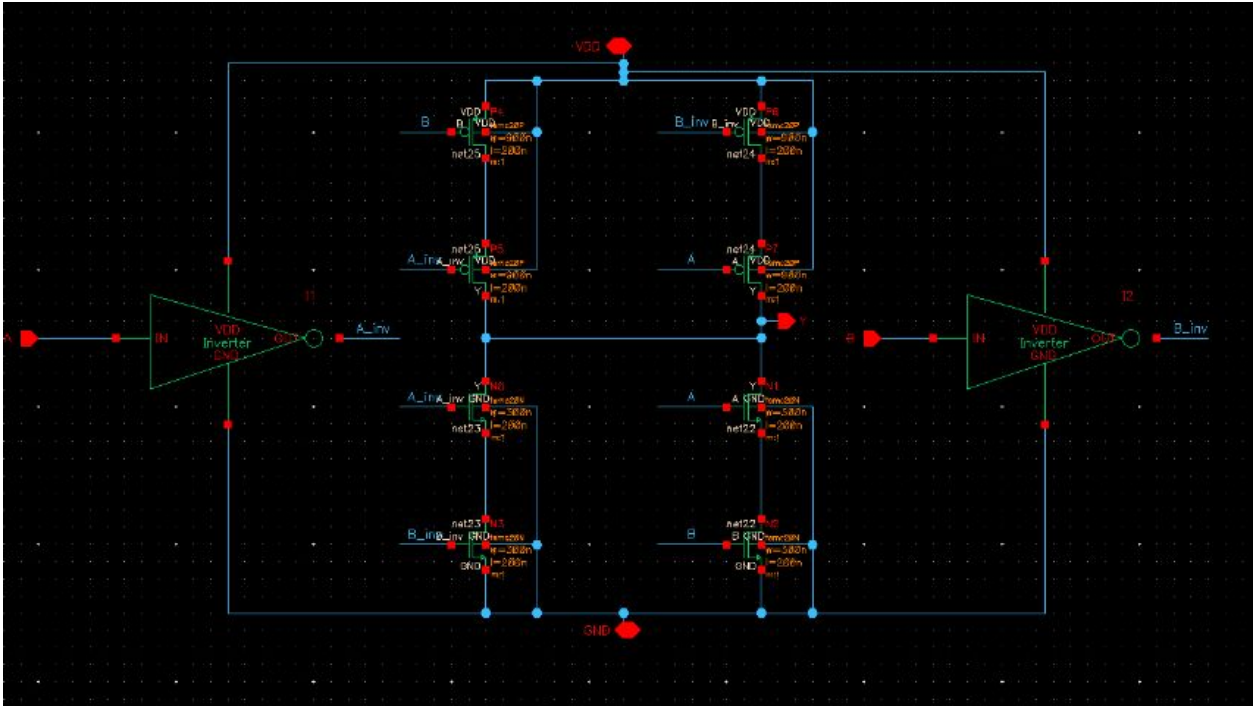


XOR Symbol

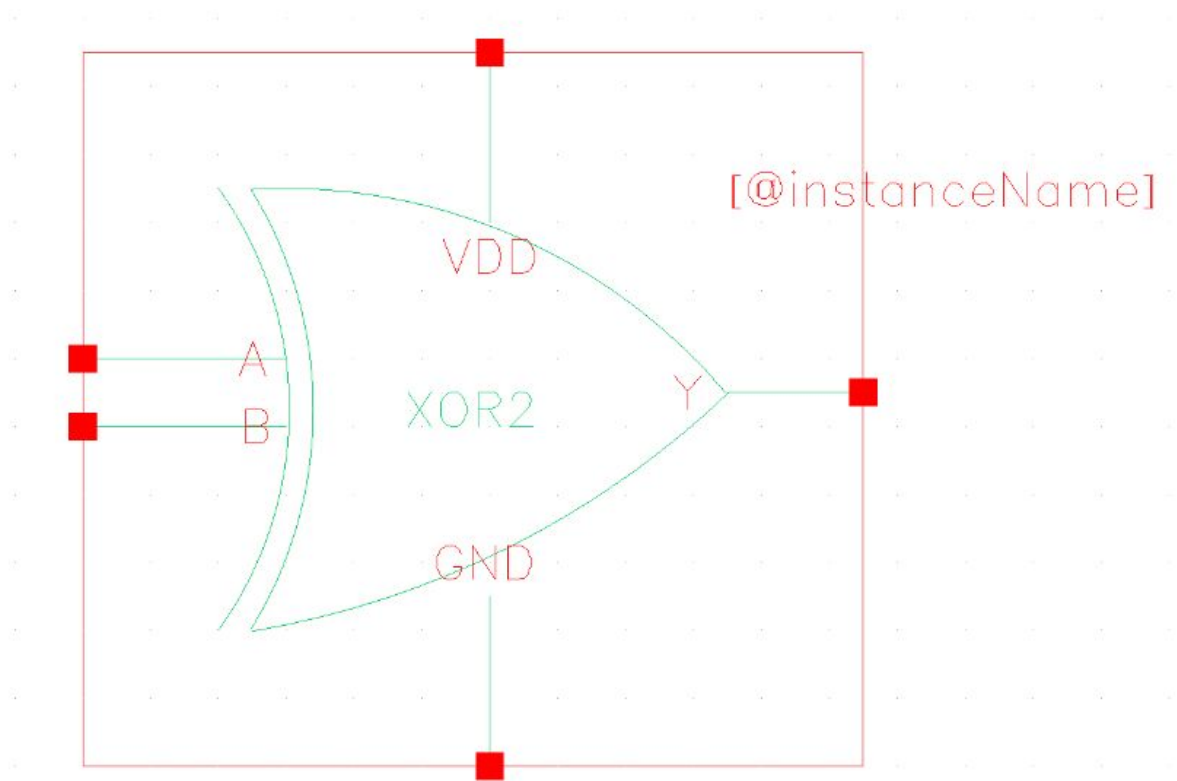

XOR Layout

 

XOR Extracted

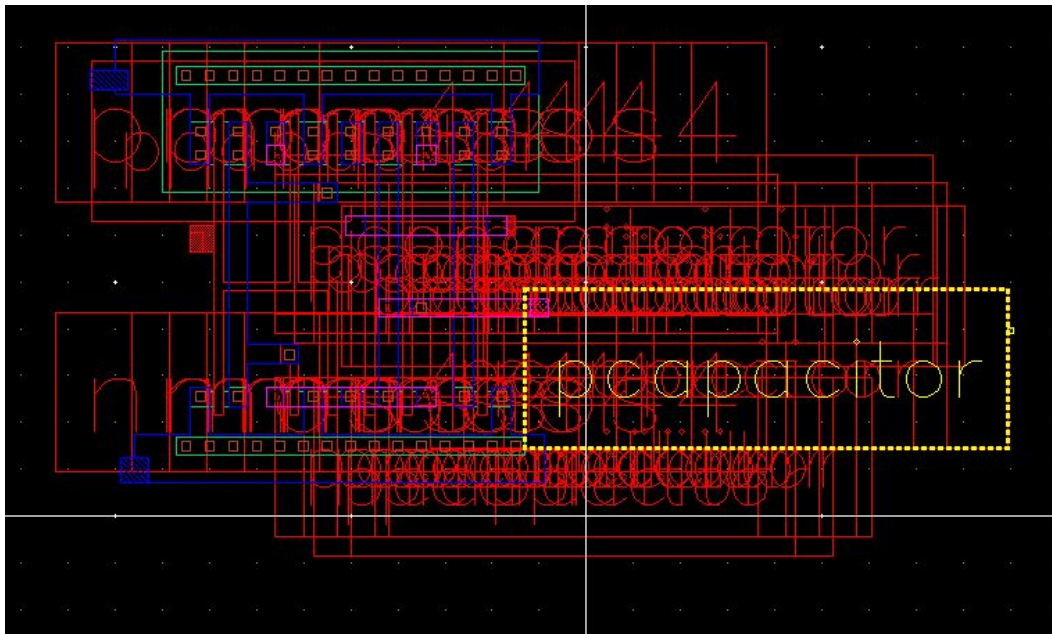

XOR LVS output file

```
Command line: /opt/coe/cadence/IC618/tools.lnx86/dfii/bin/64bit/LVS -dir /home/ugrads/k/khoadiep/LVS -l -s -t /home/ugrads/k/khoadiep/LVS/layout /home/ugrads/k/khoadiep/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.
Compiling DIVE LVS rules...

Net-list summary for /home/ugrads/k/khoadiep/LVS/layout/netlist
count
11      nets
5       terminals
6       pmos
6       nmos

Net-list summary for /home/ugrads/k/khoadiep/LVS/schematic/netlist
count
11      nets
5       terminals
6       pmos
6       nmos

Terminal correspondence points
N12     N3      A
N11     N6      B
N10     N10     GND
N13     N5      VDD
N9      N8      Y

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.

              layout schematic
              instances
un-matched    0      0
rewired       0      0
size errors   0      0
pruned        0      0
active        12     12
total         12     12

              nets
un-matched    11     11
merged        0      0
pruned        0      0
active        11     11
total         11     11
```