
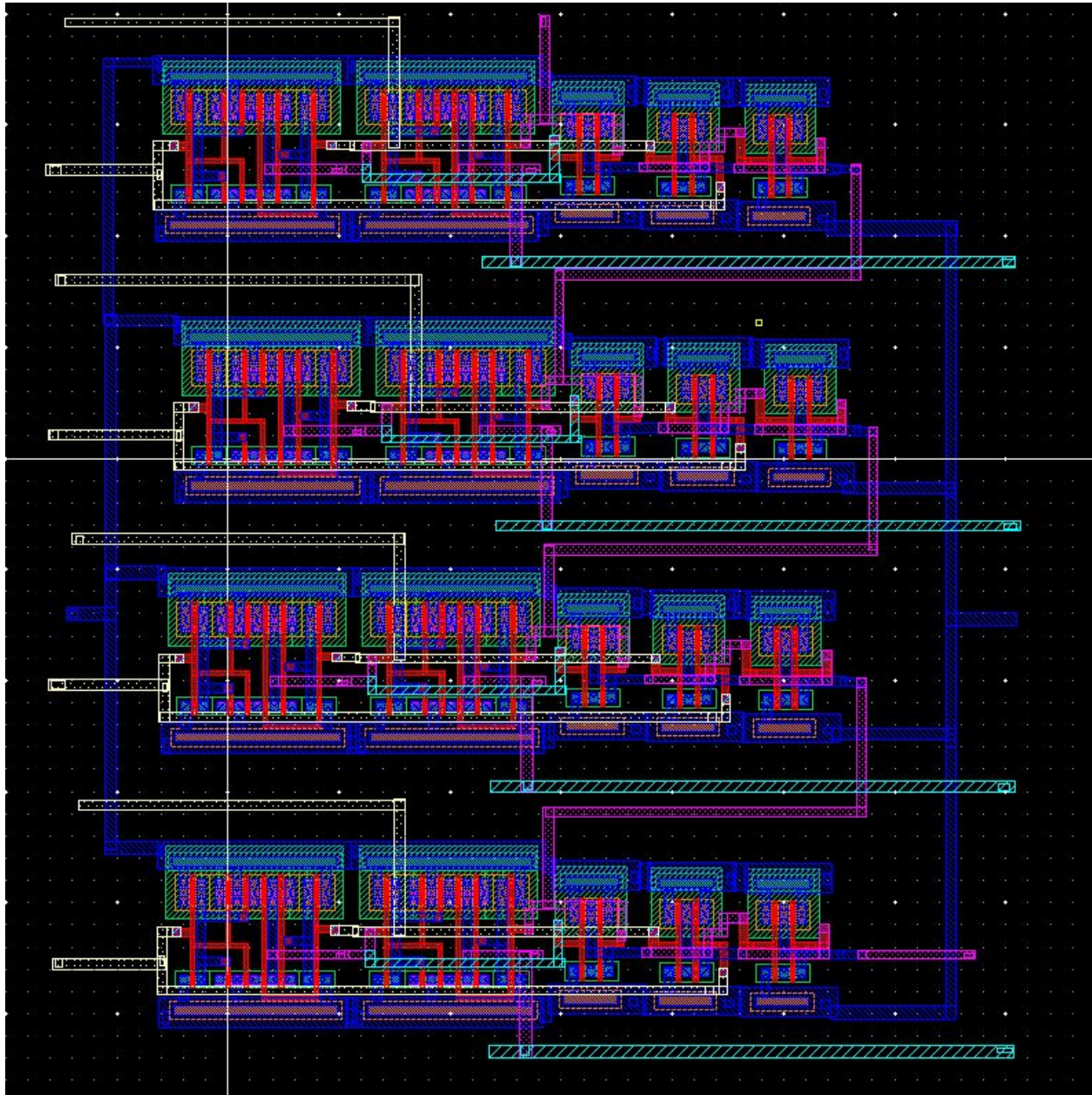


4-bit adder layout

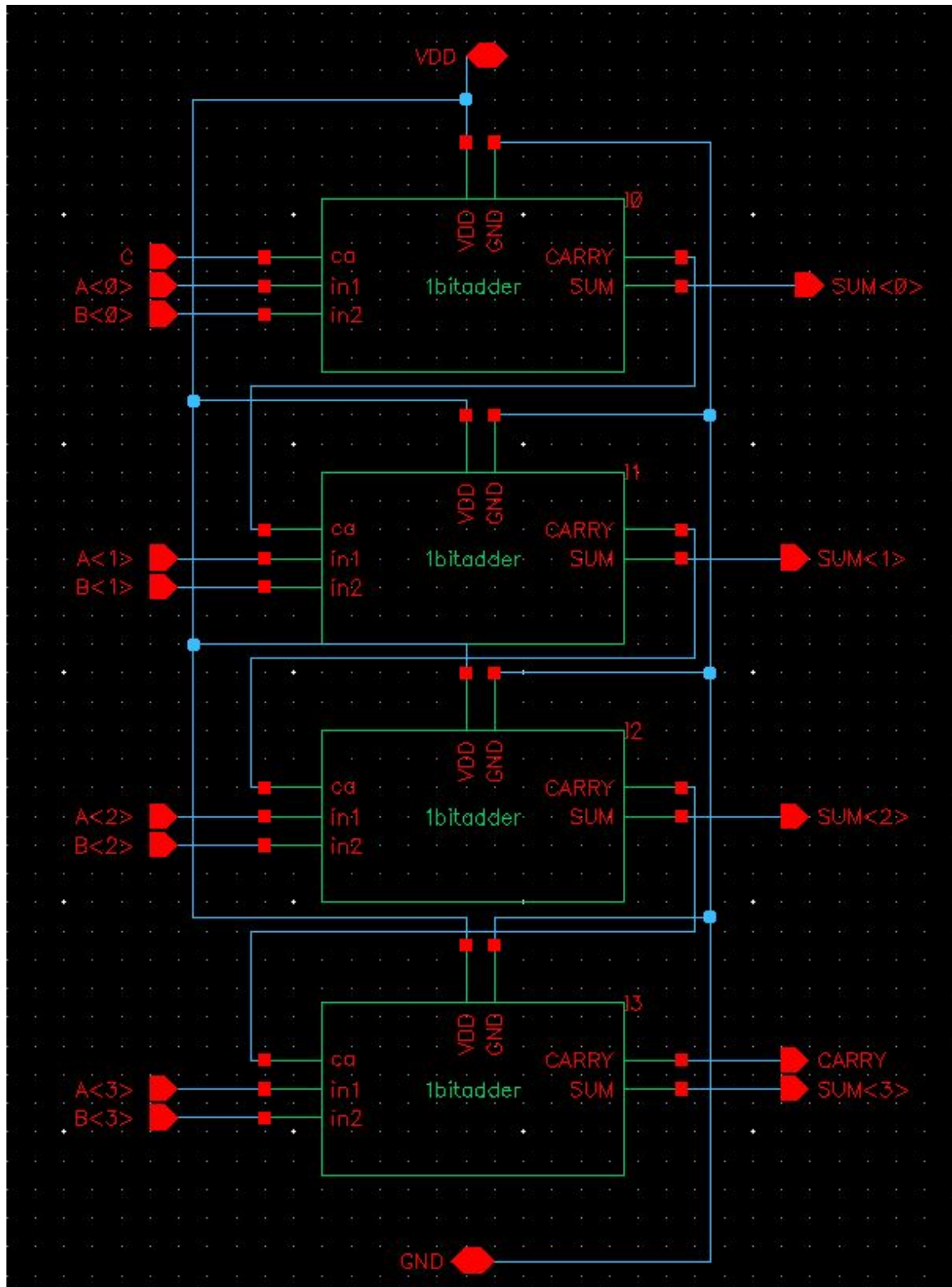

4-bit adder schematic



LVS

```
Net-list summary for /home/ugrads/k/khoadiep/cadence/LVS/schematic/netlist
count
  91          nets
  16          terminals
  72          pmos
  72          nmos
```

Terminal correspondence points

N83	N11	A<0>
N80	N7	A<1>
N77	N1	A<2>
N75	N8	A<3>
N90	N2	B<0>
N87	N16	B<1>
N86	N6	B<2>
N85	N5	B<3>
N81	N9	C
N89	N18	CARRY
N78	N4	GND
N84	N13	SUM<0>
N82	N10	SUM<1>
N79	N3	SUM<2>
N76	N12	SUM<3>
N88	N14	VDD

Devices in the netlist but not in the rules:
pcapacitor

Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	144	144
total	144	144
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	91	91
total	91	91


Rising Delays:

Input	Sum0	Sum1	Sum2	Sum3	Carry
0000/1111/1	0.4199	0.6159	0.8212	1.02248	0.9074
1010/0101/0	0.4237	0.6547	0.6691	0.6642	0.3603
1010/0101/1	0.4467	0.6595	0.6243	0.7511	0.3154
1100/1000/0	0.4709	0.6615	0.5942	0.8456	0.3604


Falling Delays:

Input	Sum0	Sum1	Sum2	Sum3	Carry
0000/1111/1	0.4316	0.6162	0.7994	0.9864	0.9739
1010/0101/0	0.4384	0.6663	0.6334	0.6359	0.3324
1010/0101/1	0.4542	0.6424	0.6304	0.7246	0.3843
1100/1000/0	0.4718	0.6346	0.6260	0.8425	0.3342


A = 0000, B = 1111, Carry In = 1

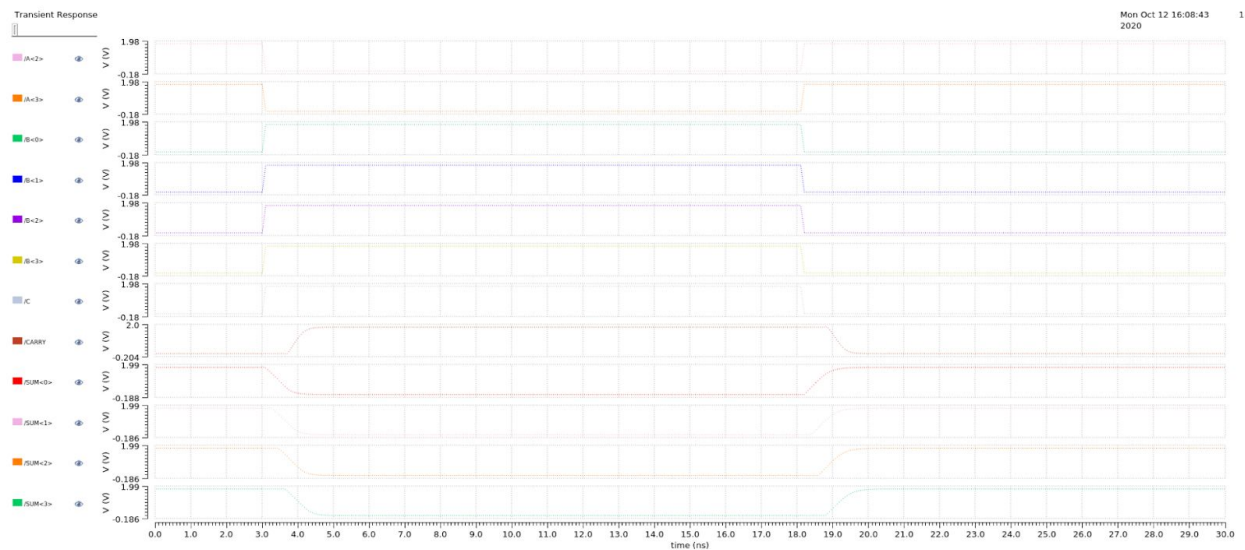


A = 1010, B = 0101, Carry In = 0

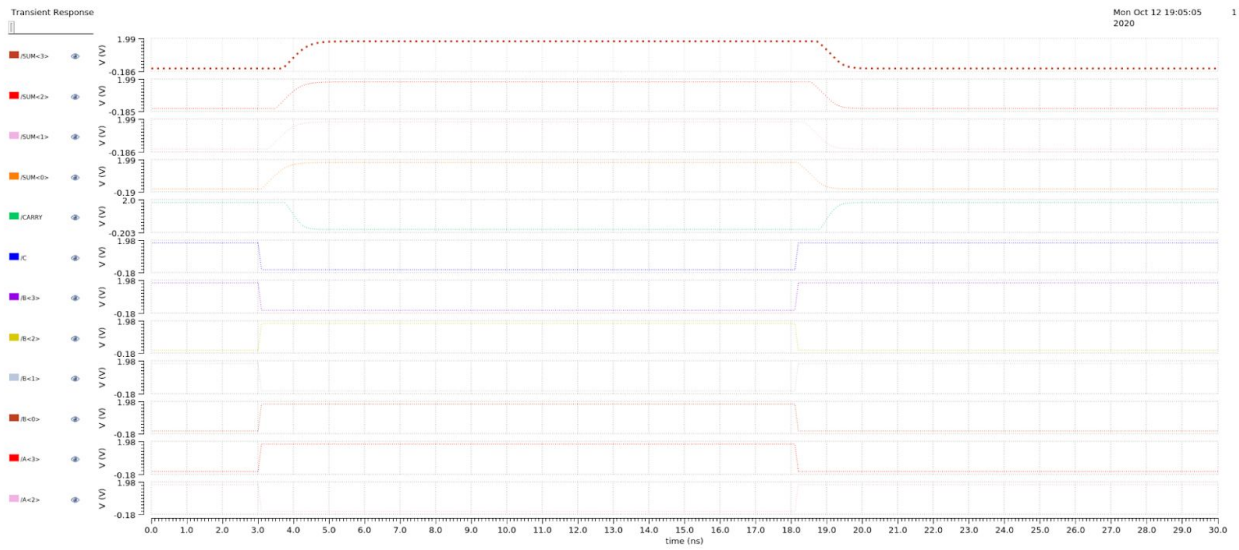

A = 1010, B = 0101, Carry In = 1

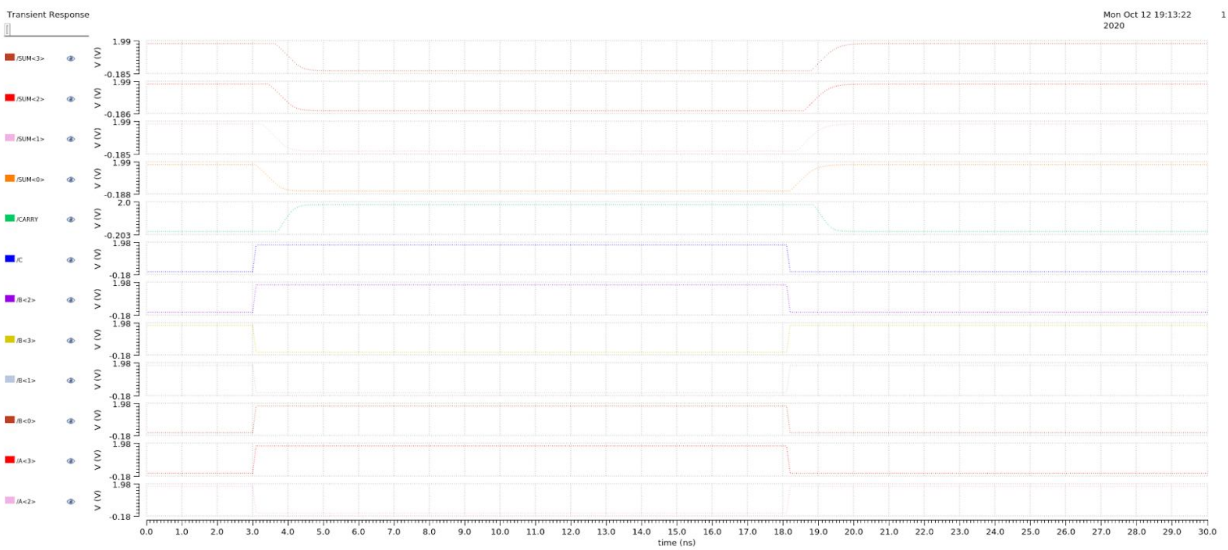

A = 1100, B = 1000, Carry In = 0

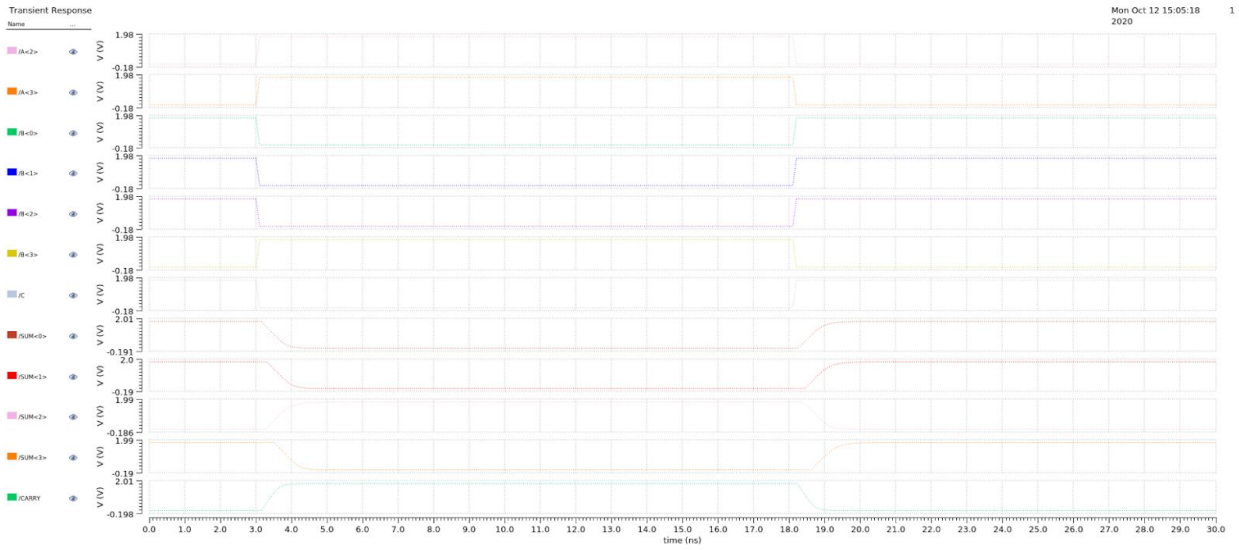

Power Dissipations

A	B	Carry In	Voltage Source	Value
0000	1111	1	VDD	-55.99E-6
1010	0101	0	VDD	-56.91E-6
1010	0101	1	VDD	-55.99E-6
1100	1000	0	VDD	-57.09E-6